

ENGR 378 Digital Systems Design

Exp. 5: Keyboard Interface

Submitted by:

Björn Franzén
Kristian Lauszus

Oct. 16, 2014

Demonstration.....	____/5
Report: Presentation	____/2
Problem analysis.....	____/2
Design work.....	____/5
Results.....	____/5
Conclusion/Discussion.....	____/1
Total.....	____/ 20

Problem Analysis

In this lab we needed to read the input from a keyboard and output it to four 7-segment displays. Our approach to modularize it according to the picture shown in our pre-lab report.

Hardware Design

We decided to create two modules, one for interpreting data from the keyboard and one top-module for displaying the transmission value on the 7-segment display.

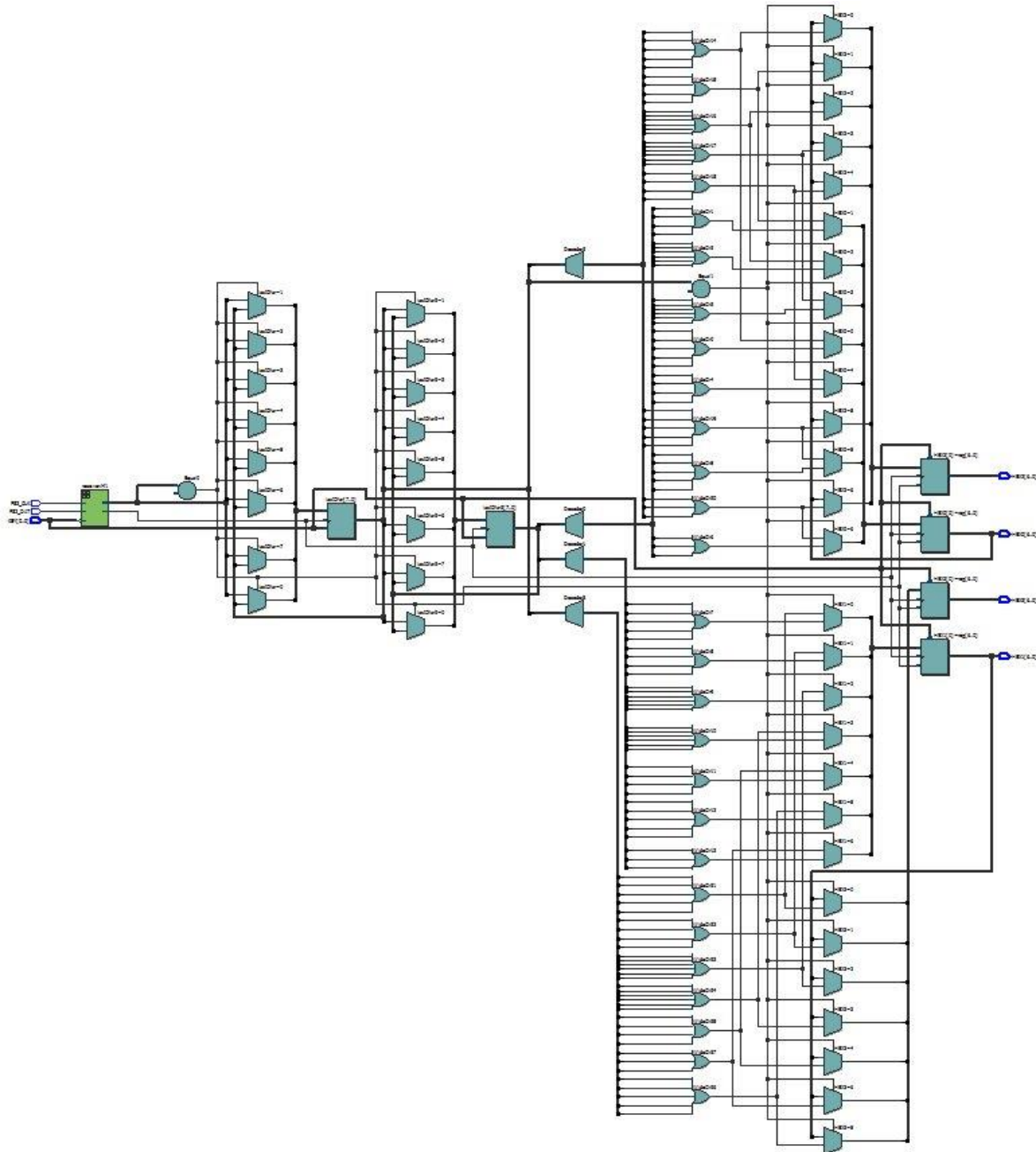


Figure 1 – Hardware synthesis of the top module.

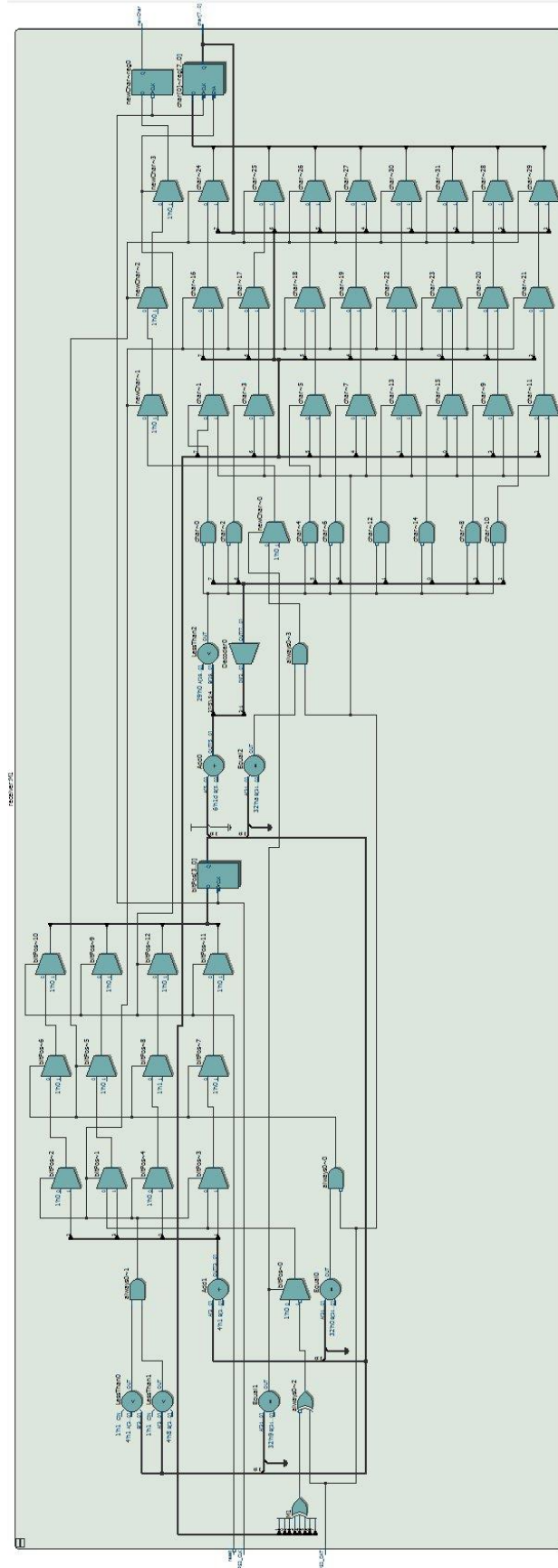


Figure 2 - Hardware synthesis of the receiver module.

Verilog Modelling

The receiver module consists of one always statement that is triggered on a negative edge on the PS/2 clock signal. The basic implementation is a state machine where the state is determined by the current position in the transmission sequence. First it checks that the start bit is high, then it reads the following 8-bits into a buffer and checks the parity afterwards. Finally it checks the stop-bit. If all passes it will indicate that a new transmission is received by setting an output high.

The top-module will trigger on the positive edge of this output and checks for the stop sequence. If true then it will shift the last transmission in from the right, on the 7-segment displays. There is a special case when pressing the arrow keys, as these send out two transmissions instead of one, as described in the lab manual. We solved this by checking for the special character, 0xE0, that indicates a 16-bit key-code. If that happens it will show the first transmission on the two rightmost displays and 0xE0 on the two leftmost displays.

Finally we implemented a reset signal that clears the displays and resets the receiver module.

Results/Verification

First we created a test bench to verify that our receiver module worked as expected. The test bench simulated an arbitrary transmission of 0x55. The waveform can be seen in Figure 3.

After we confirmed the receiver module, we wrote a test bench for the entire design. We did this by simulating a release of the “up arrow” key. As can be seen in Figure 4, everything worked as expected.



Figure 3 - Simulation waveform of the receiver module.


 


Figure 4 - Simulation waveform of entire design.

Conclusions and Discussion

We found that it was good to have a slightly larger project this time so that we could break down the design into different parts and divide the work between us. This actually created fewer problems for us, in relation to previous labs and allowed us to do this entire lab during one session.

Pre-lab

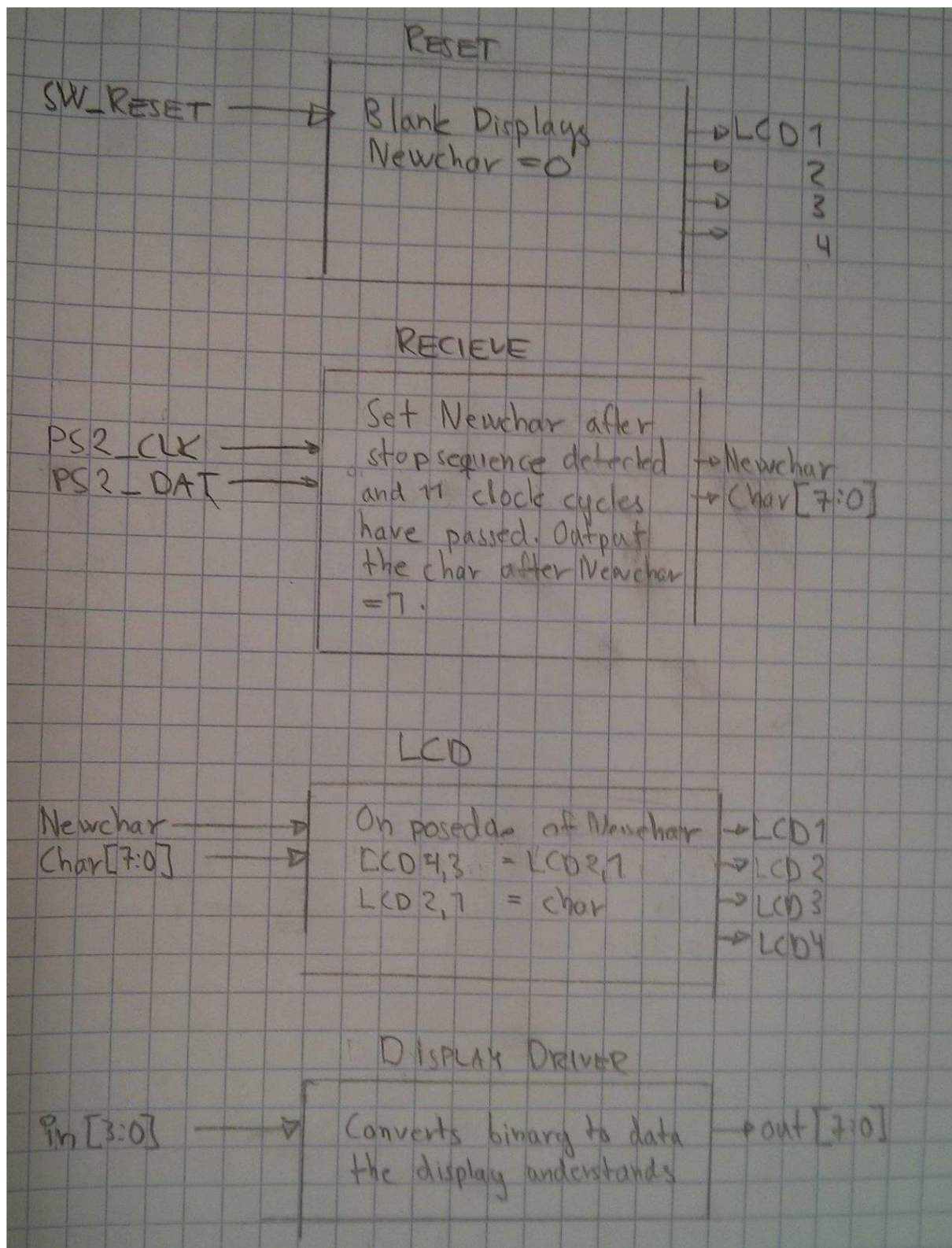

Work Breakdown

The receiver module was created by Kristian and the top module by Björn.

HDL Source Code

```
module keyboard(  
    output reg [6:0] HEX0, HEX1, HEX2, HEX3, // 7-segment displays  
    input  PS2_CLK, PS2_DAT, // The clock and data signals from the PS/2 device  
    input [0:0] KEY // Used as reset signal  
);  
  
    wire newChar;  
    wire [7:0] char;  
    reg [7:0] lastChar, lastChar2;  
  
    receiver M1(.newChar(newChar), .char(char), .PS2_CLK(PS2_CLK),  
        .PS2_DAT(PS2_DAT), .reset(!KEY[0]));  
  
    always @ (posedge newChar or negedge KEY[0]) begin  
        if (!KEY[0]) begin  
            HEX0 = 7'b1111111; // OFF  
            HEX1 = 7'b1111111; // OFF  
            HEX2 = 7'b1111111; // OFF  
            HEX3 = 7'b1111111; // OFF  
  
            end  
            else if (char == 8'hF0) begin // This will ensure that we only  
display the last value once the button is released  
                if (lastChar == 8'hE0) begin // Make sure that it display  
the entire key-code of the arrows and other buttons that sends a 16-bit  
transmission  
  
                    HEX2 = display_driver(lastChar[3:0]);  
                    HEX3 = display_driver(lastChar[7:4]);  
                    HEX0 = display_driver(lastChar2[3:0]);  
                    HEX1 = display_driver(lastChar2[7:4]);  
  
                    end  
                    else begin  
                        HEX2 = HEX0; // Shift value to next two displays  
                        HEX3 = HEX1;  
                        HEX0 = display_driver(lastChar[3:0]);  
                        HEX1 = display_driver(lastChar[7:4]);  
  
                        end  
                    end  
                    else begin  
                        lastChar2 = lastChar; // Save the char before last char  
                        lastChar = char; // Save last char  
  
                        end  
                    end  
  
                end  
  
            function [6:0] display_driver;  
                input [3:0] in;  
                case (in)  
                    4'b0000 : display_driver = 7'b1000000; // 0  
                    4'b0001 : display_driver = 7'b1111001; // 1  
                    4'b0010 : display_driver = 7'b0100100; // 2  
                    4'b0011 : display_driver = 7'b0110000; // 3  
                    4'b0100 : display_driver = 7'b0011001; // 4  
                    4'b0101 : display_driver = 7'b0010010; // 5  
                    4'b0110 : display_driver = 7'b0000011; // 6  
                    4'b0111 : display_driver = 7'b1111000; // 7  
                    4'b1000 : display_driver = 7'b0000000; // 8  
                    4'b1001 : display_driver = 7'b0011000; // 9  
  
                    4'b1010 : display_driver = 7'b0001000; // A  
                    4'b1011 : display_driver = 7'b0000000; // B (8)  
                    4'b1100 : display_driver = 7'b1000110; // C  
                    4'b1101 : display_driver = 7'b1000000; // D (0)  
                    4'b1110 : display_driver = 7'b0000110; // E  
                    4'b1111 : display_driver = 7'b0001110; // F  
  
                    default : display_driver = 7'b1111111; // OFF  
  
                endcase  
            endfunction
```

```

endmodule

module t_keyboard;
    wire [6:0] HEX0, HEX1, HEX2, HEX3; // 7-segment displays
    reg PS2_CLK, PS2_DAT; // The clock and data signals from the PS/2 device
    reg reset; // Used as reset signal

    keyboard M1(.PS2_CLK(PS2_CLK), .PS2_DAT(PS2_DAT), .KEY(reset), .HEX0(HEX0),
    .HEX1(HEX1), .HEX2(HEX2), .HEX3(HEX3));

    initial begin
        PS2_CLK = 1; reset = 1; // Set initial values
    end

    always #5 PS2_CLK = !PS2_CLK; // Generate clk signal

    // Test by releasing up arrow
    always begin
        reset = 0;
        #10 reset = 1;

        // Send 0x75
        PS2_DAT = 0; // Start bit
        #10 PS2_DAT = 1; // D0
        #10 PS2_DAT = 0; // D1
        #10 PS2_DAT = 1; // D2
        #10 PS2_DAT = 0; // D3
        #10 PS2_DAT = 1; // D4
        #10 PS2_DAT = 1; // D5
        #10 PS2_DAT = 1; // D6
        #10 PS2_DAT = 0; // D7
        #10 PS2_DAT = 0; // Parity bit
        #10 PS2_DAT = 1; // Stop bit

        // Send E0
        #50 PS2_DAT = 0; // Start bit
        #10 PS2_DAT = 0; // D0
        #10 PS2_DAT = 0; // D1
        #10 PS2_DAT = 0; // D2
        #10 PS2_DAT = 0; // D3
        #10 PS2_DAT = 0; // D4
        #10 PS2_DAT = 1; // D5
        #10 PS2_DAT = 1; // D6
        #10 PS2_DAT = 1; // D7
        #10 PS2_DAT = 0; // Parity bit
        #10 PS2_DAT = 1; // Stop bit

        // Send F0
        #50 PS2_DAT = 0; // Start bit
        #10 PS2_DAT = 0; // D0
        #10 PS2_DAT = 0; // D1
        #10 PS2_DAT = 0; // D2
        #10 PS2_DAT = 0; // D3
        #10 PS2_DAT = 1; // D4
        #10 PS2_DAT = 1; // D5
        #10 PS2_DAT = 1; // D6
        #10 PS2_DAT = 1; // D7
        #10 PS2_DAT = 1; // Parity bit
        #10 PS2_DAT = 1; // Stop bit

        #50 reset = 0;
        #10 $stop;
    end

end

endmodule

module receiver(
    output reg newChar,

```

```

        output reg[7:0] char,
        input PS2_CLK, PS2_DAT, reset
    );
    reg[3:0] bitPos; // Current bit position in transmission
    wire parityCheck;

    xor M1(parityCheck, char[0], char[1], char[2], char[3], char[4], char[5],
char[6], char[7]);

    always @ (negedge PS2_CLK)
    begin
        newChar = 0;
        if (reset) bitPos = 0; // Reset bit position
        else if (bitPos == 0 & PS2_DAT == 0) bitPos = 1; // Check start
bit
        else if (bitPos >= 1 & bitPos <= 8) begin
            char[bitPos - 1] = PS2_DAT;
            bitPos = bitPos + 1'd1;
        end
        else if (bitPos == 9) begin // Check parity
            if (PS2_DAT == ~parityCheck)
                bitPos = 10; // Go to stop bit state
            else
                bitPos = 0; // Error in transmission
        end
        else if (bitPos == 10 & PS2_DAT == 1) begin // Check stop bit
            newChar = 1;
            bitPos = 0;
        end
        else bitPos = 0; // If everything fails, then there must be an
error in the transmission
    end

endmodule

module t_receiver;
    wire newChar;
    wire [7:0] char;
    reg PS2_CLK, PS2_DAT, reset;

    receiver M1(.newChar(newChar), .char(char), .PS2_CLK(PS2_CLK),
.PS2_DAT(PS2_DAT), .reset(reset));

    initial begin
        PS2_CLK = 1; reset = 0; // Set initial values
    end

    always #5 PS2_CLK = !PS2_CLK; // Generate clk signal

    always begin
        reset = 1;
        #10 reset = 0;
        PS2_DAT = 0; // Start bit
        #10 PS2_DAT = 1; // D0
        #10 PS2_DAT = 0; // D1
        #10 PS2_DAT = 1; // D2
        #10 PS2_DAT = 0; // D3
        #10 PS2_DAT = 1; // D4
        #10 PS2_DAT = 0; // D5
        #10 PS2_DAT = 1; // D6
        #10 PS2_DAT = 0; // D7
        #10 PS2_DAT = 1; // Parity bit
        #10 PS2_DAT = 1; // Stop bit
        #10 $stop;
    end

end

endmodule

```